

Maciej Girek  
HW 2  
CS 362  
02/08/2018

1. Convert the following decimal numbers to their 32-bit signed binary representation. Use two's complement to represent negative numbers.

- a) 1000110110111001
- b) 0110010000011110
- c) 1110101010101100
- d) 1111101100011111

2. For each of the following cases, determine whether the addition of the two numbers given would cause an overflow. Assume all numbers are signed and stored as 4-bit binary numbers

- a) 4 and 5 - overflow
- b) 4 and -5 no overflow
- c) -2 and 6 no overflow
- d) -5 and -3 no overflow

3. Determine the total current ( $I_{\text{total}}$ ) flowing in the circuits given below

- a)  $I_{\text{total}} = I_1 + I_2$   
 $I_1 = V/R_1 = 9/900 = 1/100 \text{ A}$   
 $I_2 = V/R_2 = 9/900 = 1/100 \text{ A}$   
 $I_{\text{total}} = 1/50 \text{ A}$
- b)  
 $I_{\text{total}} = 5/250 = 1/50 \text{ A}$

4. Determine if the sentences (a) to (d) are True/False by analyzing the circuit given below.

- a) False
- b) False
- c) True
- d) True

5. Write the truth table for the CMOS Circuit given below and mention what logic gate does it represent.

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Therefore the table represents the NAND gate